




Measure the voltage between the common ground and the point where R4,R6 R8 and R10 meet, set the voltage to the calculated value by adjusting VR1

Measure the voltage when the PIR is clear

Them measure the voltage when its

Lets Say Vclear =1volt

activated Valarm = 4 volts

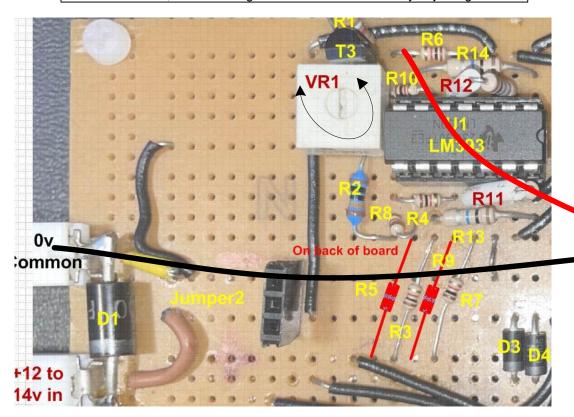

Vref